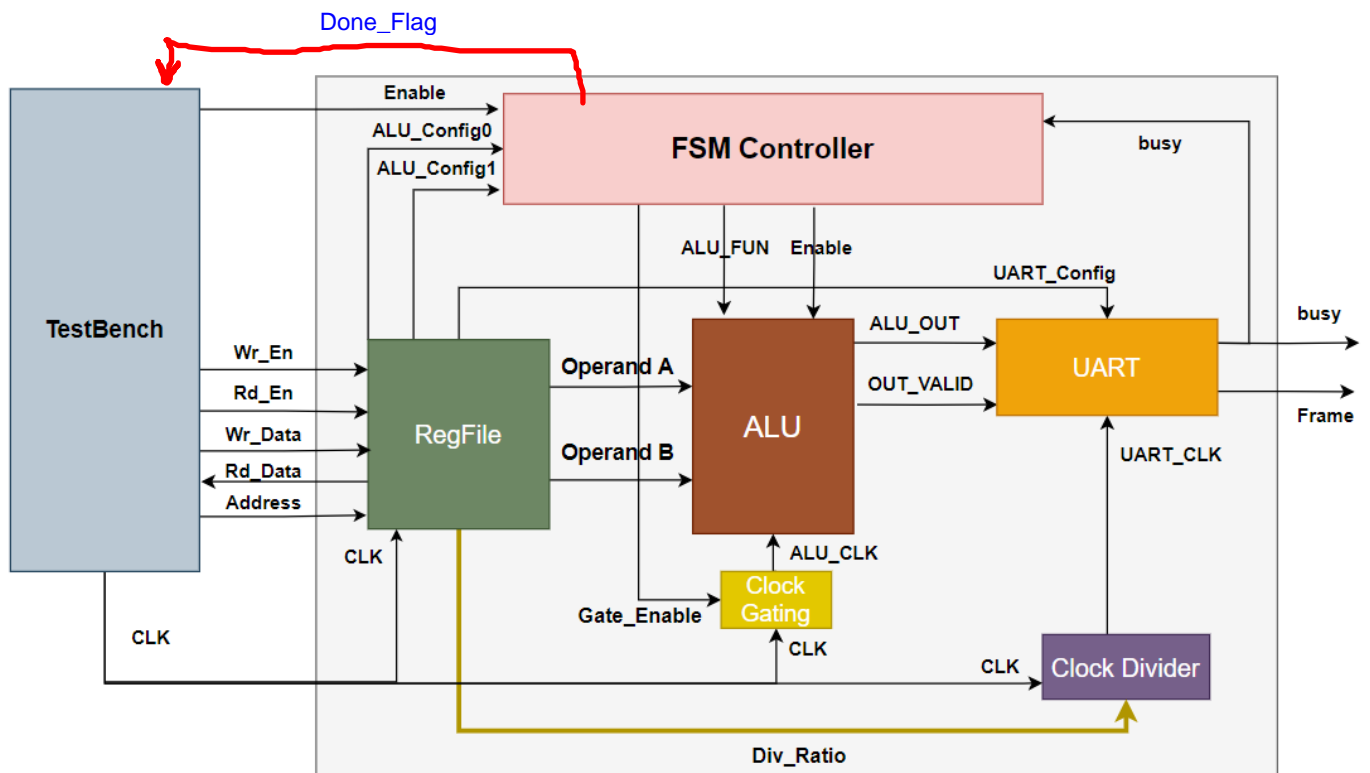


# Final System

## Introduction: -

- This System Is Our Final Target: -




- Description: -

- This system contains 6 blocks: -
  - RegFile
  - ALU
  - UART
  - FSM Controller
  - Clock Divider
  - Clock Gating

## 1) RegFile: -

- Block Interface: -**

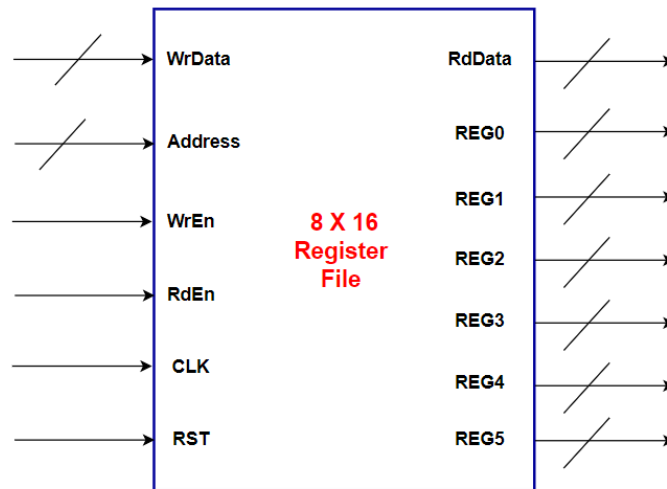

- Signal Description: -**

Port	Direction	Width	Description	Connected to
<b>CLK</b>	IN	1	Clock Signal	TOP Input Port
<b>RST</b>	IN	1	Active Low Async Reset	TOP Input Port
<b>Address</b>	IN	Parameterized (default : 4 bits)	Address bus	TOP Input Port
<b>WrEn</b>	IN	1	Write Enable	TOP Input Port
<b>RdEn</b>	IN	1	Read Enable	TOP Input Port
<b>WrData</b>	IN	Parameterized (default : 8 bits)	Write Data Bus	TOP Input Port
<b>RdData</b>	OUT	Parameterized (default : 8 bits)	Read Data Bus	TOP output Port
<b>REG0</b>	OUT	Parameterized (default : 8 bits)	Register at Address 0x0	ALU (A)
<b>REG1</b>	OUT	Parameterized (default : 8 bits)	Register at Address 0x1	ALU (B)
<b>REG2</b>	OUT	Parameterized (default : 8 bits)	Register at Address 0x2	FSM Controller (ALU Config0)
<b>REG3</b>	OUT	Parameterized (default : 8 bits)	Register at Address 0x3	FSM Controller (ALU Config1)
<b>REG4</b>	OUT	Parameterized (default : 8 bits)	Register at Address 0x4	UART (UART_Config)
<b>REG5</b>	OUT	Parameterized (default : 8 bits)	Register at Address 0x5	Clock Divider (Div_Ratio)

- **Reserved Registers Description: -**

1) REG0 (**Address: 0x0**)

ALU Operand A

2) REG1 (**Address: 0x1**)

ALU Operand B

3) REG2 (**Address: 0x2**)

ALU Config0

1. Each bit value represents enable certain ALU function in case of value = **"1"** and disable the function in case of value = **"0"**

REG2[0]: **Arithmetic Adding**

REG2[1]: **Arithmetic Subtraction**

REG2[2]: **Arithmetic Multiplication**

REG2[3]: **Arithmetic Division**

REG2[4]: **Logical AND**

REG2[5]: **Logical OR**

REG2[6]: **Logical NAND**

REG2[7]: **Logical NOR**

4) REG3 (**Address: 0x3**)

ALU Config1

2. Each bit value represents enable certain ALU function in case of value = **"1"** and disable the function in case of value = **"0"**

REG3[0]: **Logical XOR**

REG3[1]: **Logical XNOR**

REG3[2]: **CMP (A = B)**

REG3[3]: **CMP (A > B)**

REG3[4]: **CMP (A < B)**

REG3[5]: **Shift (A >> 1)**

REG3[6]: **Shift (A << 1)**

REG3[7]: **No Operation**

5) REG4 (**Address: 0x4**)

UART Config
-------------

REG4[0]: **Parity Enable**

REG3[1]: **Parity Type**

REG3[2:7]: **Not Used**

6) REG5 (**Address: 0x5**)

Div Ratio
-----------

REG5[0:3]: **Division ratio**


REG3[4:7]: **Not Used**

### Modifications: -

3. Refer to Assignment 4.2, you need to add the following registers as **outputs** on the Register File interface: -
  - 1) Register at address 0x0 on port REG0
  - 2) Register at address 0x1 on port REG1
  - 3) Register at address 0x2 on port REG2
  - 4) Register at address 0x3 on port REG3
  - 5) Register at address 0x4 on port REG4
  - 6) Register at address 0x5 on port REG5

## 2) ALU:

- Block Interface: -

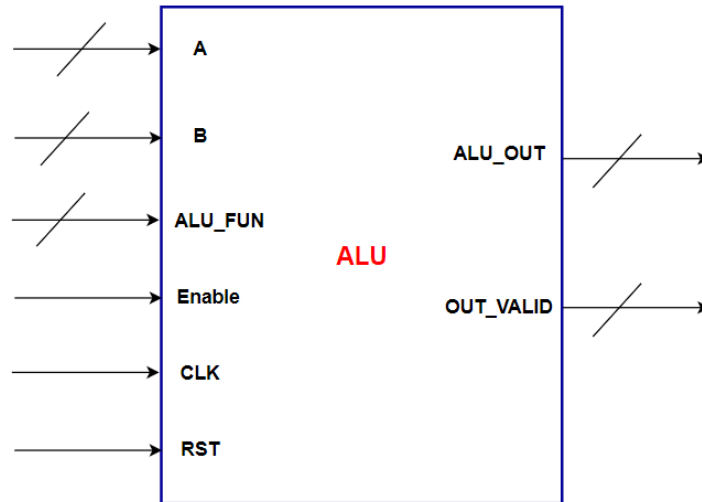

- Signal Description: -


Port	Direction	Width	Description	Connected to
CLK	IN	1	Clock Signal	TOP Input Port
RST	IN	1	Active Low Async Reset	TOP Input Port
A	IN	Parameterized (default : 8 bits)	Operand A	RegFile (REG0)
B	IN	Parameterized (default : 8 bits)	Operand B	RegFile (REG1)
ALU_FUN	IN	Parameterized (default : 4 bits)	ALU Function	FSM Controller (ALU_FUN)
Enable	IN	1	ALU Enable	FSM Controller (ALU_Enable)
ALU_OUT	OUT	Parameterized (default : 8 bits)	ALU Result	UART (P_DATA)
OUT_VALID	OUT	1	Result Valid	UART (DATA_VALID)

## Modifications: -

4. Refer to Assignment 3, you need to add the following modifications: -
  1. Replace all the flags (Arith\_flag, Logic\_flag, CMP\_flag, Shift\_flag) by **OUT\_VALID** signal
  2. All the outputs (ALU\_OUT, OUT\_VALID) are registered
  3. Add Enable signal,
    - when Activated (Enable = 1'b1)
      - ALU\_OUT = result of the operation
      - VALID\_OUT = 1'b1
    - when deactivated
      - ALU\_OUT = 0
      - VALID\_OUT = 0

### 3) UART: -

- Block Interface: -**

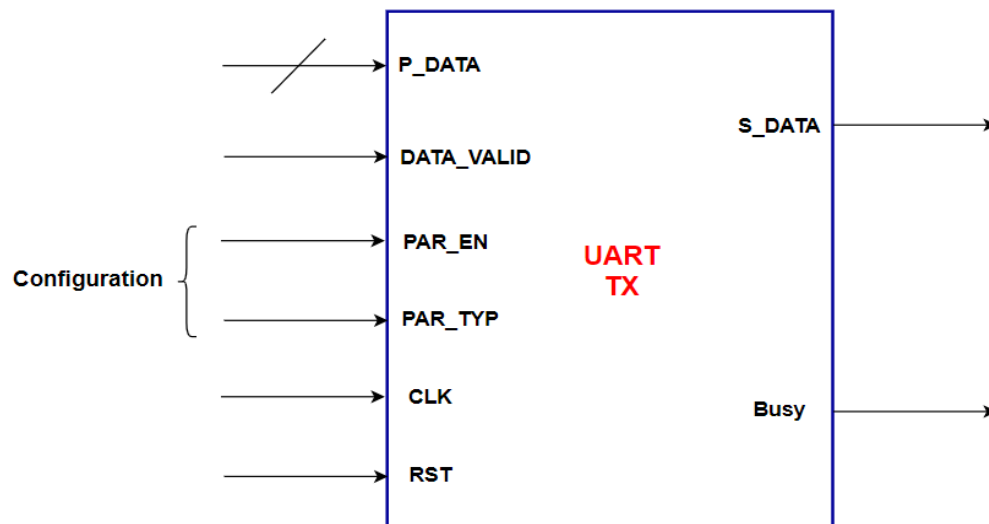


- Signal Description: -**

Port	Direction	Width	Description	Connected to
<b>CLK</b>	IN	1	Clock Signal	TOP Input Port
<b>RST</b>	IN	1	Active Low Async Reset	TOP Input Port
<b>PAR_EN</b>	IN	1	Parity Enable	RegFile (UART_Config[0])
<b>PAR_TYP</b>	IN	1	Parity Type	RegFile (UART_Config[1])
<b>P_DATA</b>	IN	Parameterized (default : 8 bits)	Parallel IN Data	ALU (ALU_OUT)
<b>DATA_VALID</b>	IN	1	IN Data Valid	ALU (OUT_VALID)
<b>S_DATA</b>	OUT	1	frame serial bits	TOP Output Port
<b>Busy</b>	OUT	1	Uart status signal	1) TOP Output Port 2) FSM Controller (UART_Status)

**No Modifications is needed**

#### 4) Clock Divider: -

- **Block Interface: -**

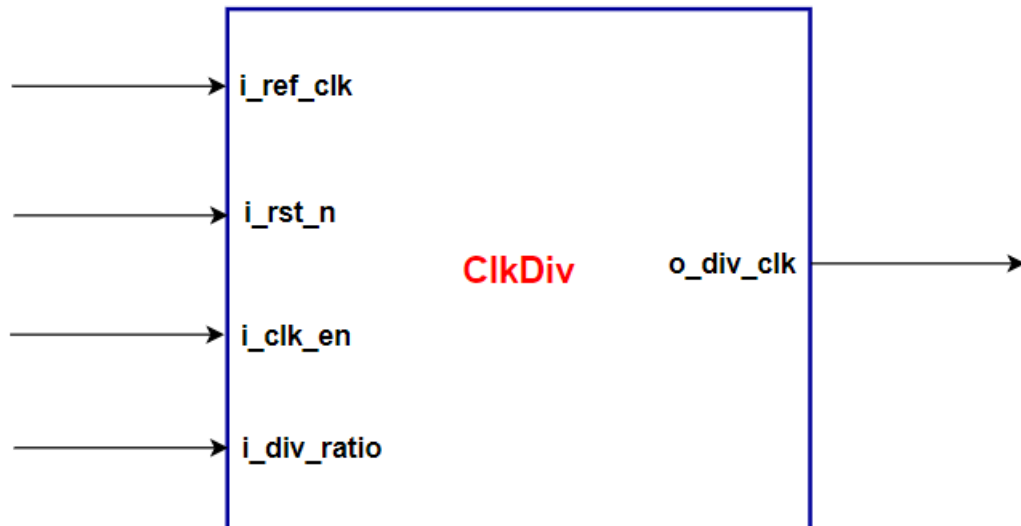

- **Signal Description: -**


Port	Direction	Width	Description	Connected to
I_ref_clk	IN	1	Clock Signal	TOP Input Port
I_rst_n	IN	1	Active Low Async Reset	TOP Input Port
I_clk_en	IN	1	Clock divider enable	TOP Input Port
I_div_ratio	IN	Parameterized (default : 4 bits)	Division ratio	RegFile (Div_Ratio)
O_div_clk	out	1	Divided clock	UART (CLK)

**No Modifications is needed**



## 5) Clock Gating: -

- **Block Interface: -**

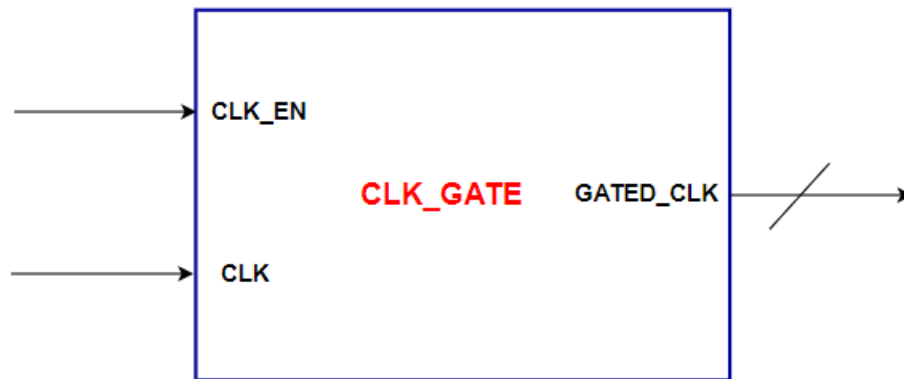


- **Signal Description: -**

Port	Direction	Width	Description	Connected to
CLK	IN	1	Clock Signal	TOP Input Port
CLK_EN	IN	1	Clock Enable	FSM Controller (Gate_Enable)
GATED_CLK	out	1	Gated Clock signal	ALU (CLK)

**No Modifications is needed**

## 6) FSM\_Controller: -

- Block Interface: -

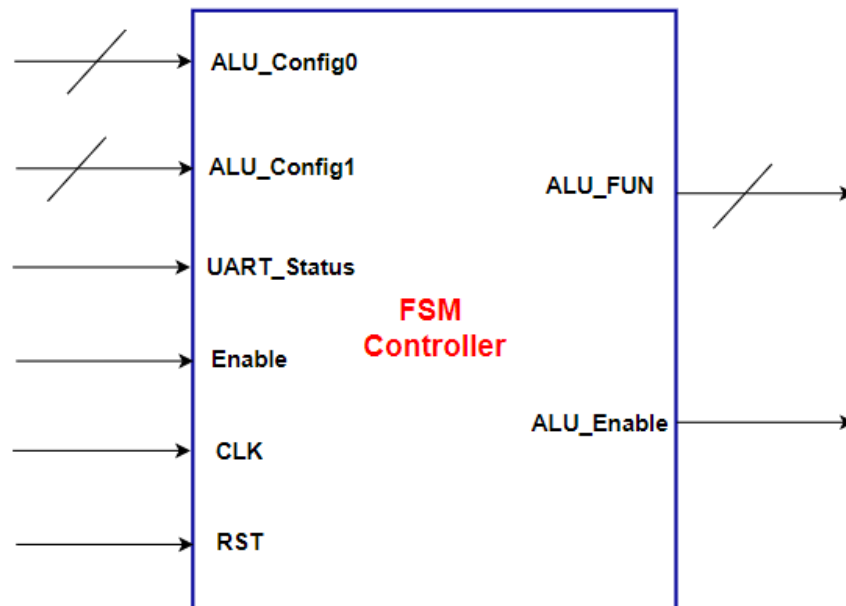

- Signal Description: -

Port	Direction	Width	Description	Connected to
CLK	IN	1	Clock Signal	TOP Input Port
RST	IN	1	Active Low Async Reset	TOP Input Port
UART_Status	IN	1	Uart status signal	UART (busy)
Enable	IN	1	Parity Type	TOP Input Port
ALU_Config0	IN	Parameterized (default : 8 bits)	ALU Configuration Register 0	ALU (ALU_OUT)
ALU_Config0	IN	Parameterized (default : 8 bits)	ALU Configuration Register 1	ALU (OUT_VALID)
ALU_FUN	OUT	Parameterized (default : 4 bits)	ALU Function signal	ALU (ALU_FUN)
ALU_Enable	OUT	1	ALU Enable signal	ALU (Enable)

## System Specifications: -

- The system need to do some ALU functions based on the values stored in **ALU\_config0** and **ALU\_Config1** registers in Register File and send the result of the ALU operation serially through UART protocol
- Minimum of ALU operations equal 0
  - (register at 0x0 = 8'h0 && register at 0x1= 8'h0)
- Maximum of ALU operations equal 16
  - (register at 0x0 = 8'hFF && register at 0x1= 8'hFF)
- Reference clock is 20 MHz
- Div\_ratio can be **3** or **6** or **8**
- Clock Divider is always on (clock divider enable = 1)

## Sequence of Operation (Must include in the testbench): -

- Initially 6 write operation is needed to write the configurations in registers from address **0x0** to **0x5**
- Initially FSM\_Controller is disabled (Enable = 0) until the write configurations registers is done
- After Write operations, the FSM\_Contrller will be enabled to enable the ALU to perform certain operation and then send the result through the UART
- While UART is processing the result, the FSM\_Controller will disable the ALU & disable ALU Clock until UART finishes and busy signal get deactivated.
- Once UART busy get deactivated, the FSM\_Controller start to enable the ALU again to perform the next operation and so on until checking all the ALU\_config0 and ALU\_Config1 bits.